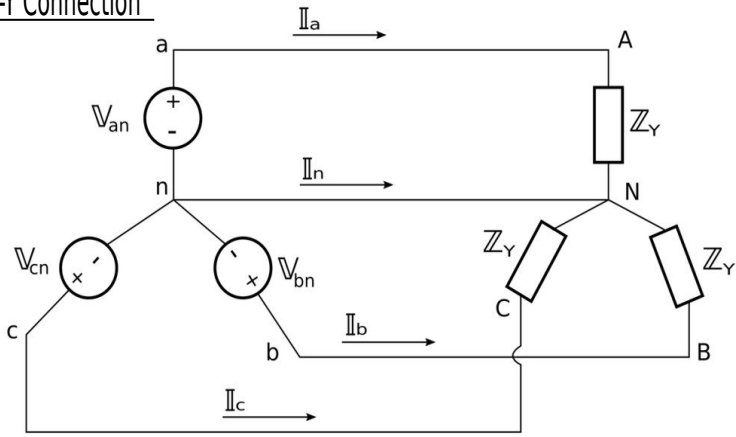


Phase and Line Voltages/Currents for three-phase systems

$V, I, Z =$ phasor (complex) expressions

Y-Y Connection



Phase Voltages:

$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle +120^\circ \end{aligned}$$

Line Voltages:

$$\begin{aligned} V_{ab} &= \sqrt{3} V_p \angle 30^\circ \\ V_{bc} &= V_{ab} \angle -120^\circ \\ V_{ca} &= V_{ab} \angle +120^\circ \end{aligned}$$


Phase Currents:

-Same as line currents

Line Currents:

$$\begin{aligned} I_a &= V_{an} / Z_Y \\ I_b &= I_a \angle -120^\circ \\ I_c &= I_a \angle +120^\circ \end{aligned}$$

Y-Delta Connection

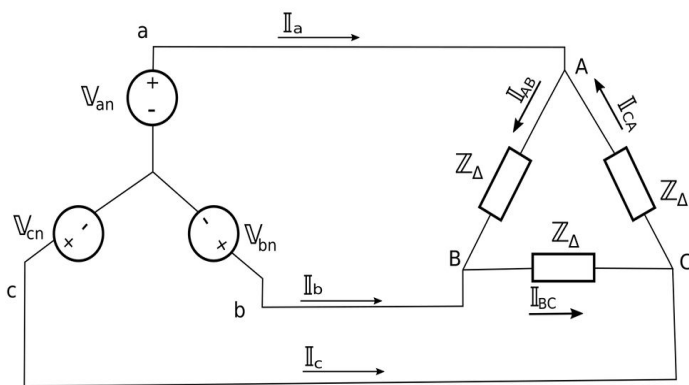

Phase Voltages:

$$\begin{aligned} V_{an} &= V_p \angle 0^\circ \\ V_{bn} &= V_p \angle -120^\circ \\ V_{cn} &= V_p \angle +120^\circ \end{aligned}$$

Line Voltages:

$$\begin{aligned} V_{ab} &= V_{AB} = \sqrt{3} V_p \angle 30^\circ \\ V_{bc} &= V_{BC} = V_{ab} \angle -120^\circ \\ V_{ca} &= V_{CA} = V_{ab} \angle +120^\circ \end{aligned}$$


Phase Currents:

$$\begin{aligned} I_{AB} &= V_{AB} / Z_\Delta \\ I_{BC} &= V_{BC} / Z_\Delta \\ I_{CA} &= V_{CA} / Z_\Delta \end{aligned}$$

Line Currents:

$$\begin{aligned} I_a &= I_{AB} \sqrt{3} \angle -30^\circ \\ I_b &= I_a \angle -120^\circ \\ I_c &= I_a \angle +120^\circ \end{aligned}$$

Delta-Delta Connection

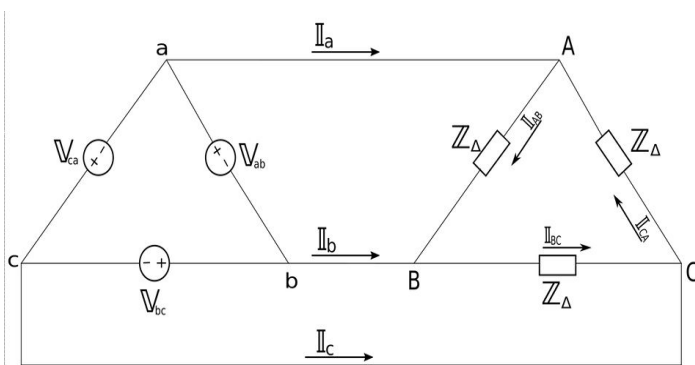

Phase Voltages:

$$\begin{aligned} V_{ab} &= V_p \angle 0^\circ \\ V_{bc} &= V_p \angle -120^\circ \\ V_{ca} &= V_p \angle +120^\circ \end{aligned}$$

Line Voltages:

-same as phase voltages


Phase Currents:

$$\begin{aligned} I_{AB} &= V_{ab} / Z_\Delta \\ I_{BC} &= V_{bc} / Z_\Delta \\ I_{CA} &= V_{ca} / Z_\Delta \end{aligned}$$

Line Currents:

$$\begin{aligned} I_a &= I_{AB} \sqrt{3} \angle -30^\circ \\ I_b &= I_a \angle -120^\circ \\ I_c &= I_a \angle +120^\circ \end{aligned}$$

Delta-Y Connection

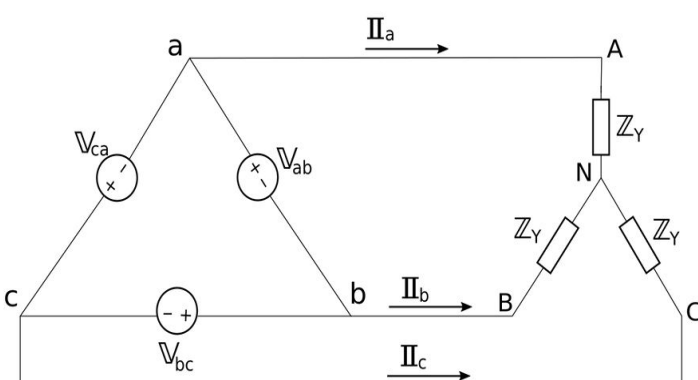

Phase Voltages:

$$\begin{aligned} V_{ab} &= V_p \angle 0^\circ \\ V_{bc} &= V_p \angle -120^\circ \\ V_{ca} &= V_p \angle +120^\circ \end{aligned}$$

Line Voltages:

-same as phase voltages

Line Currents:

$$I_a = \frac{V_p \angle -30^\circ}{\sqrt{3} Z_Y}$$

Phase Currents:

-Same as line currents

$$\begin{aligned} I_b &= I_a \angle -120^\circ \\ I_c &= I_a \angle +120^\circ \end{aligned}$$